

EL6463 Advanced Hardware Design


Lab #1

Name: Chen Shen


netID: cs5236

The screen captures of simulations

Left rotate:

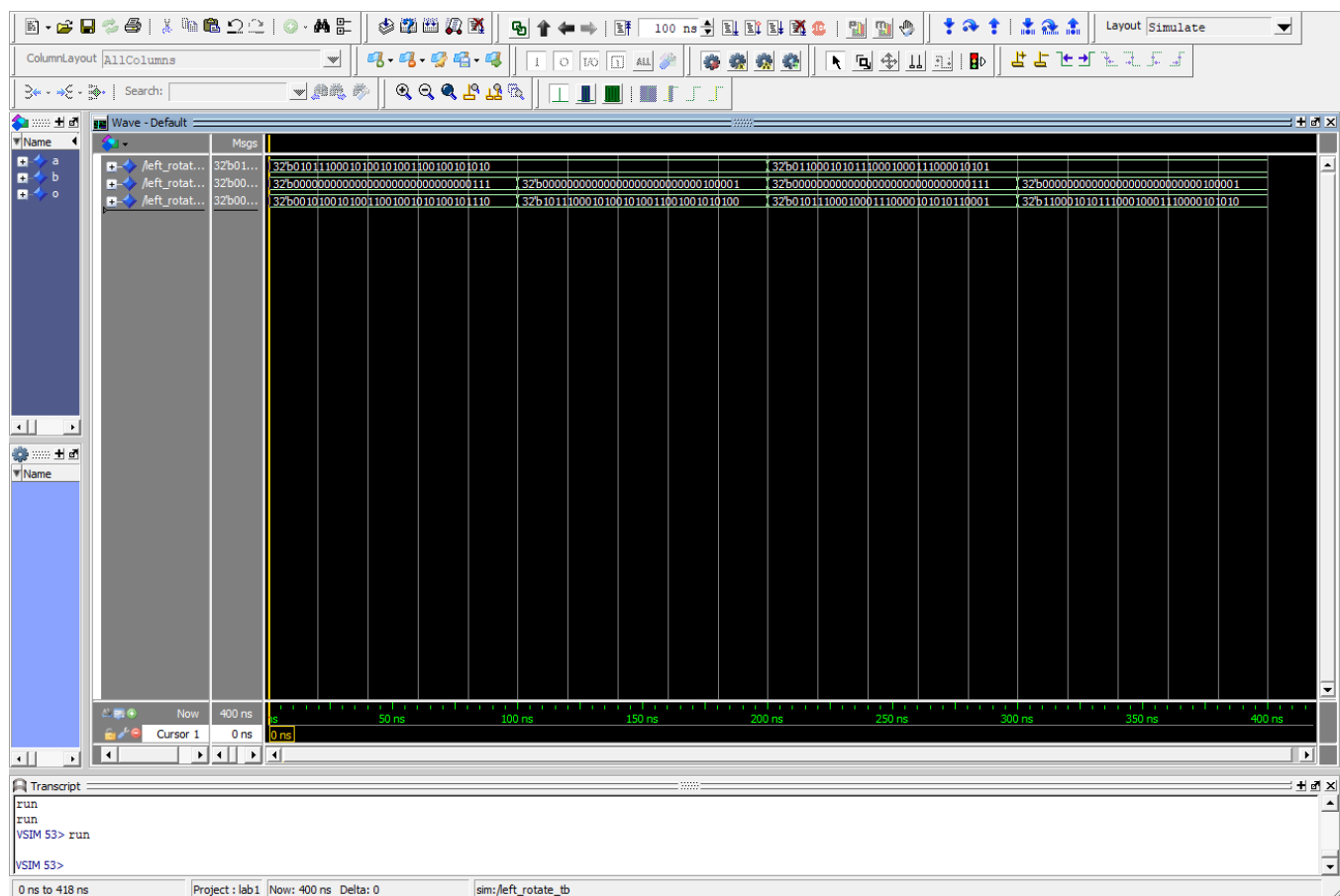


Right rotate:

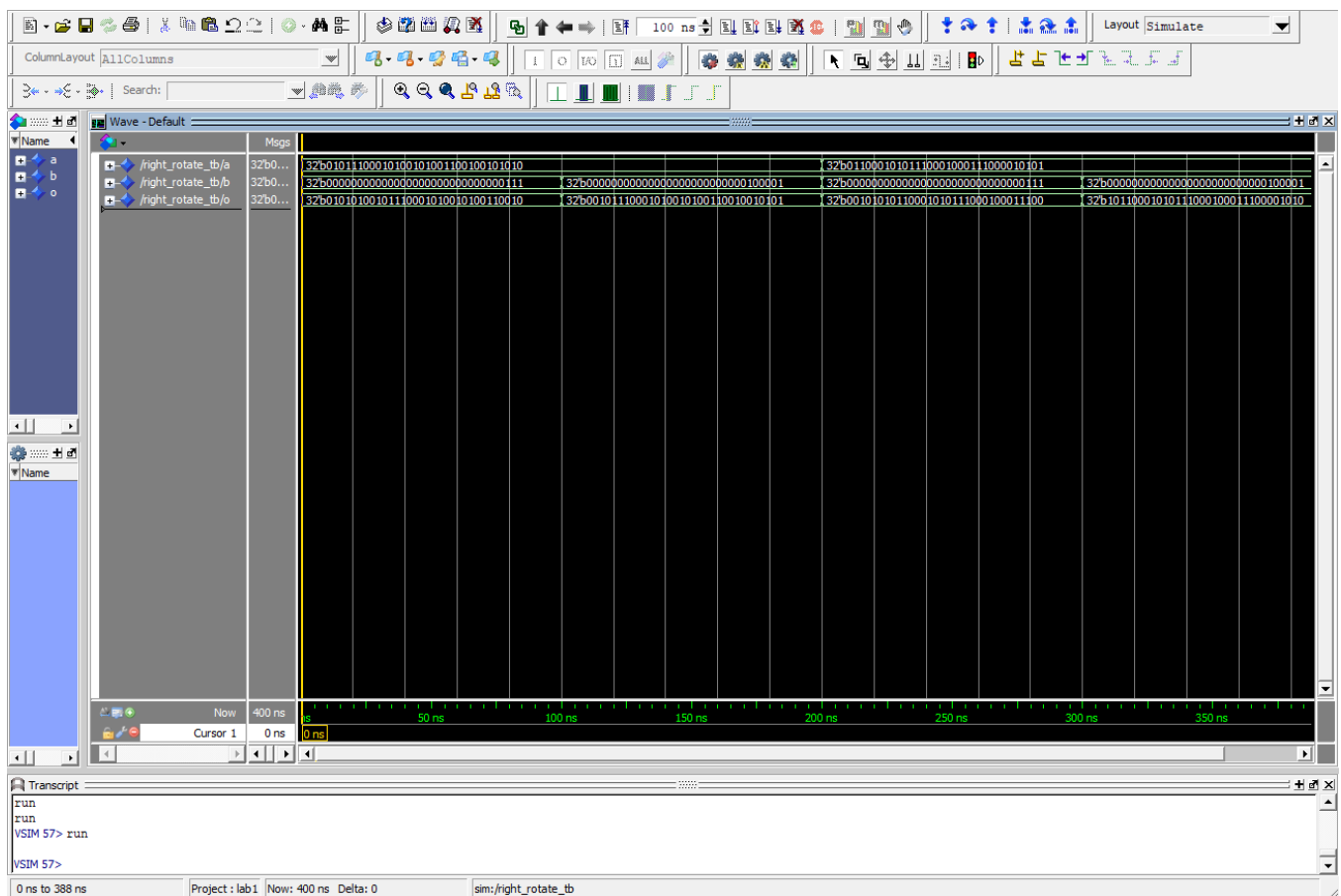


For each case, there are two values of a, 01011100010100101001100100101010 and 01100010101110001000111000010101. For each a, there are two values of b, 00000000000000000000000000000111 and 0000000000000000000000000100001. The results of simulation are shown in the figures above.

Block diagrams

Left rotate:

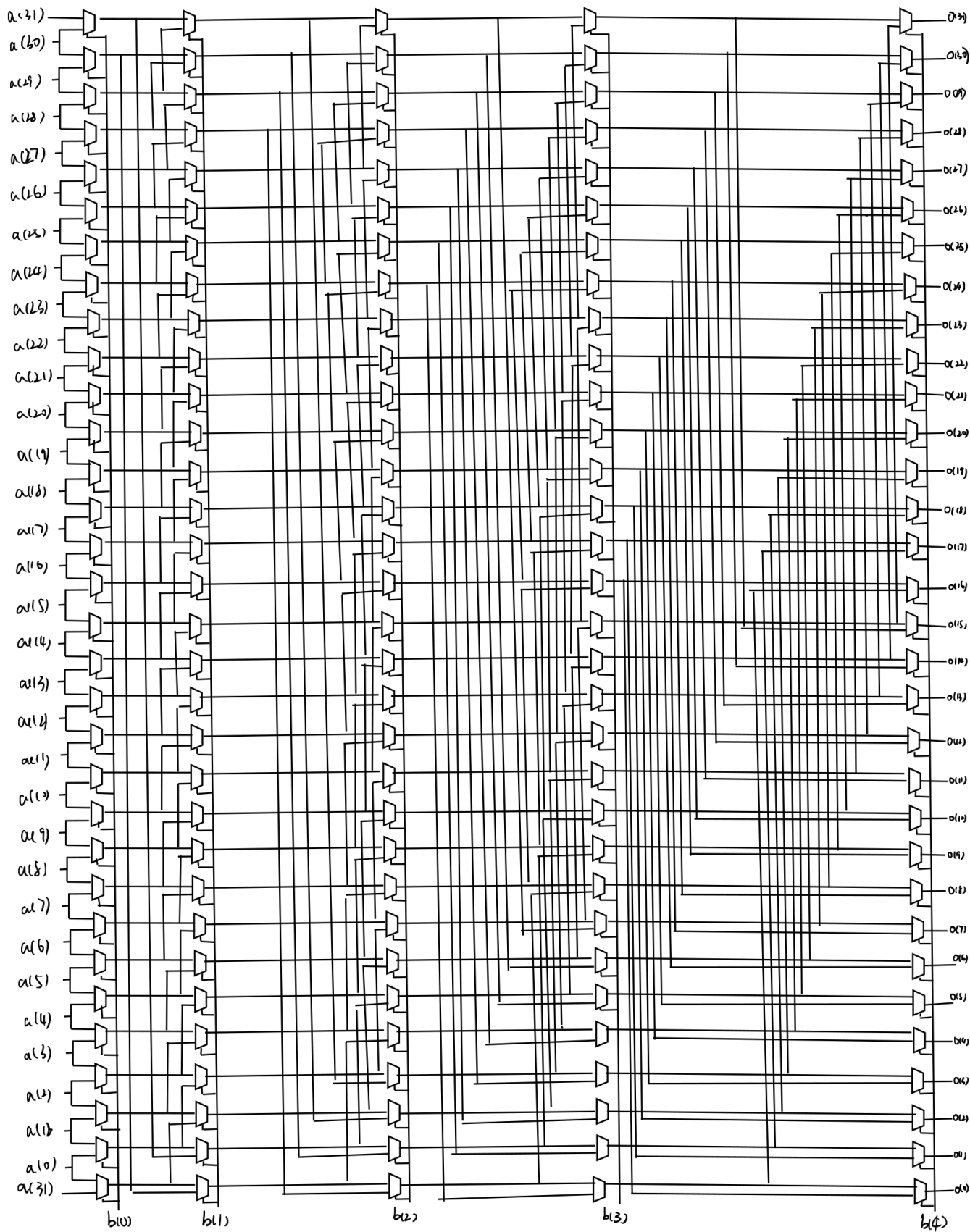

Right rotate:

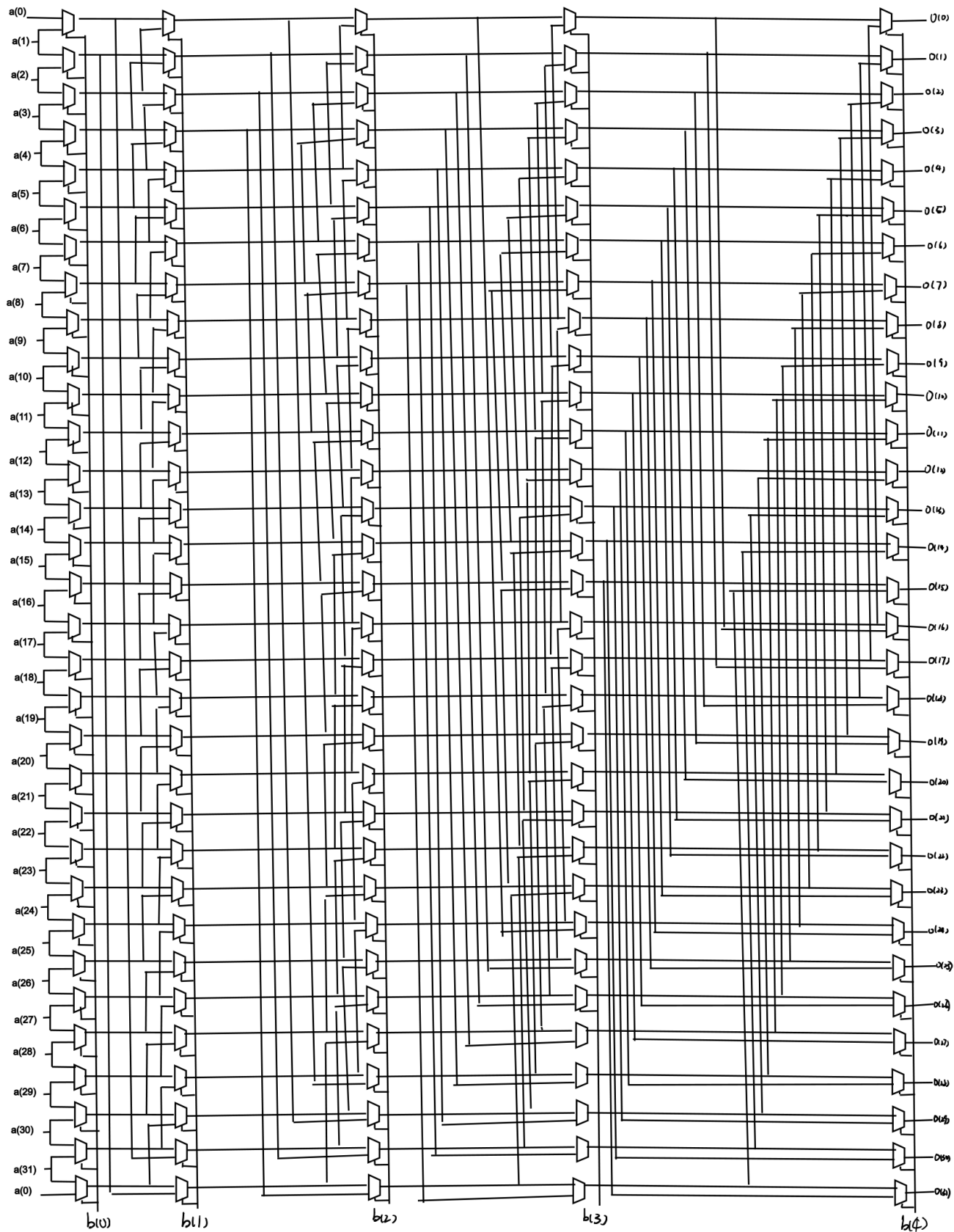

First, we can decode b into 5 different bits. For each bit, it can represent whether shift 1, 2, 4, 8, 16 bits or not. The shift bits of output can be represented by the sum of these 5 bits times the corresponding number. Thus, the general diagram is divided into 5 steps. Each step decides shift 1 bit, 2 bits, 4 bits, 8 bits, 16 bits or not. So the output o is the input a passing these 5 steps.

Hand calculation steps

For left rotate, when a is 01011100010100101001100100101010, for b equals 000000000000000000000000000000111, which is 7 in decimal, the output o should be the same as a left rotated by 7 bits. Thus, we have o supposed to be 00101001010011001001010100101110, which is the same as the result of simulation.

Besides, for b equals 000000000000000000000000000000100001, which is 33 in decimal, the output o should be the same as a left rotated by 1 bits. Thus, we have o supposed to be 10111000101001010011001001010100, which is the same as the result of simulation.

In the second case, when a is 01100010101110001000111000010101, for b equals 000000000000000000000000000000111, which is 7 in decimal, the output o should be the same as a left rotated by 7 bits. Thus, we have o supposed to be 01011100010001110000101010110001, which is the same as the result of simulation.

Besides, for b equals 000000000000000000000000000000100001, which is 33 in decimal, the output o should be the same as a left rotated by 1 bits. Thus, we have o supposed to be 11000101011100010001110000101010, which is the same as the result of simulation.

For right rotate, when a is 01011100010100101001100100101010, for b equals 000000000000000000000000000000111, which is 7 in decimal, the output o should be the same as a left rotated by 7 bits. Thus, we have o supposed to be 01010100101110001010010100110010, which is the same as the result of simulation.

Besides, for b equals 000000000000000000000000000000100001, which is 33 in decimal, the output o should be the same as a left rotated by 1 bits. Thus, we have o supposed to be 00101110001010010100110010010101, which is the same as the result of simulation.

In the second case, when a is 01100010101110001000111000010101, for b equals 000000000000000000000000000000111, which is 7 in decimal, the output o should be the same as a left rotated by 7 bits. Thus, we have o supposed to be 00101010110001010111000100011100, which is the same as the result of simulation.

Besides, for b equals 000000000000000000000000000000100001, which is 33 in decimal, the output o should be the same as a left rotated by 1 bits. Thus, we have o supposed to be 10110001010111000100011100001010, which is the same as the result of simulation.

Demo Video

<https://youtu.be/jWPMraAObeY>